

# ELEC 391

## Wind Turbine


### DEMO 3

---

A8
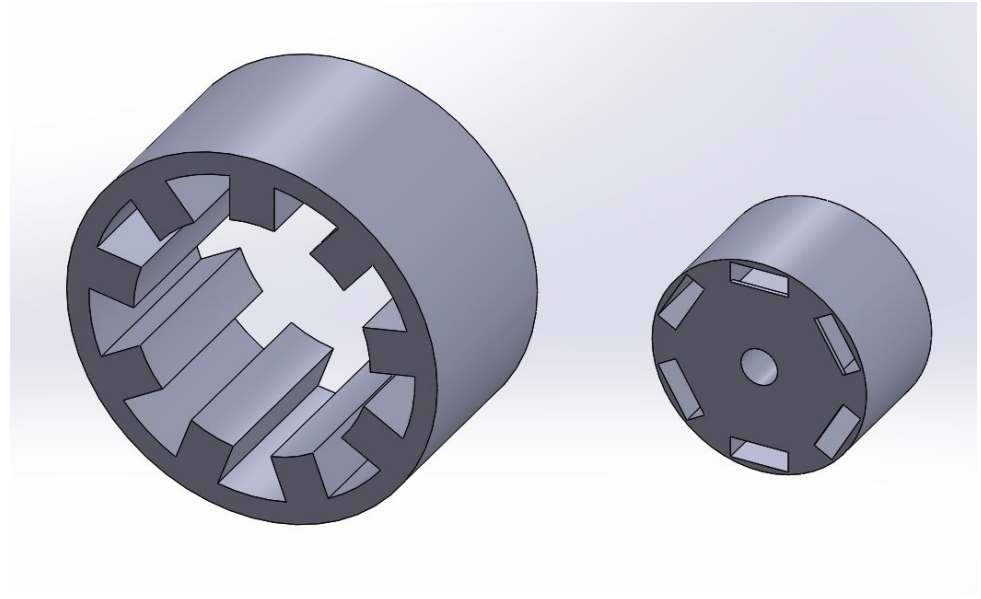
# Generator

- Permanent Magnet Synchronous Generator (PMSG)
- 6 magnetic poles (3 stacked magnets per pole, each 3158 surface Gauss)
- 9 stator poles (3 coils x 70 Turns per coil, 26 AWG)
- Reluctance per phase:  $19.25 \cdot 10^6 \text{H}^{-1}$
- 3 Ohm coil impedance per phase
- 7 V Peak per phase → 10 V through rectifier
- 600mA peak short circuit current



# Generator

## Problems:

With our topology and specifications, wiring as a motor/generator is inefficient as two coils will cancel each other out

**Solution:** Wire up as strictly a generator

High cogging torque due to small airgap resulted in an optimization problem between rotation speed and air-gap as well as torque vs speed.

**Solution:** Increase the airgap until cogging is significantly reduced. Use a 5 blade design to improve torque.



# Boost Converter



Inductor:  $\sim 100\mu\text{H}$

Mosfet: IRF540N

Diode: 20V 5A Schottky

Capacitor: 50V 1000 $\mu\text{F}$   
Electrolytic

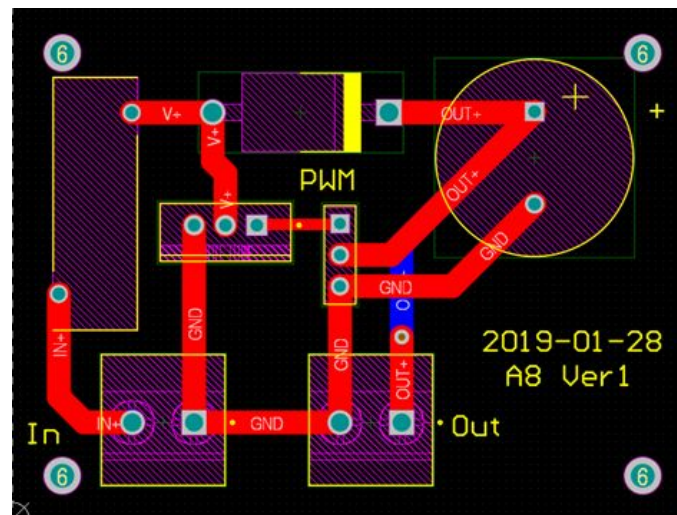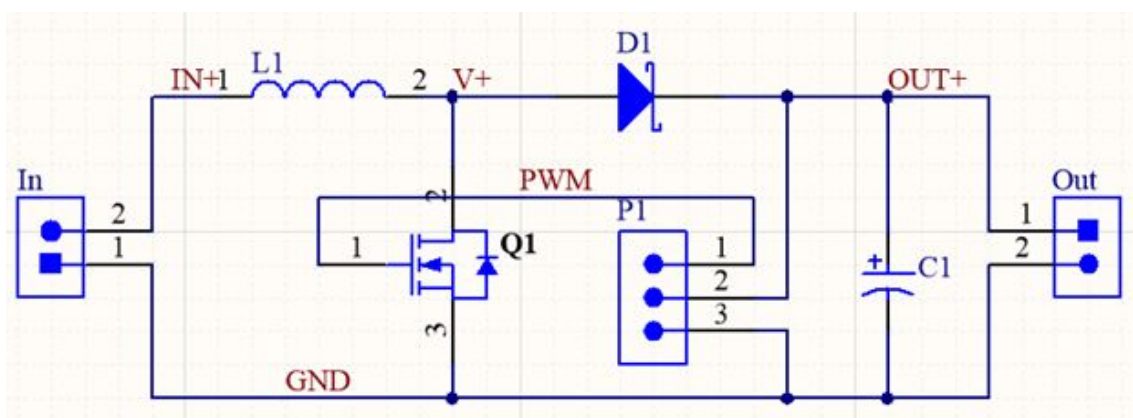Input/Output Terminals: 2 Hole  
Screw Terminal





# 3-Phase Rectifier

Diode: 20V 5A Schottky

Capacitor: 35V 3300 $\mu$ F  
Electrolytic

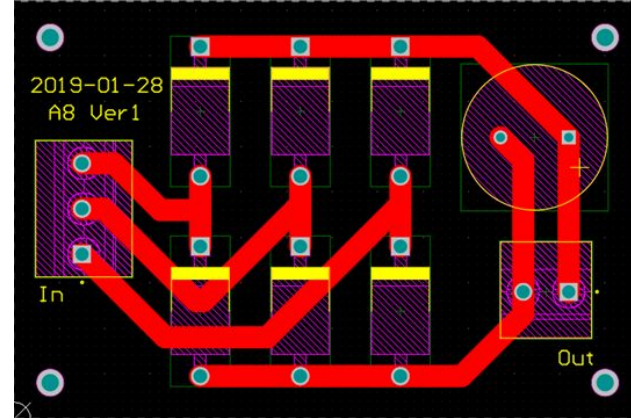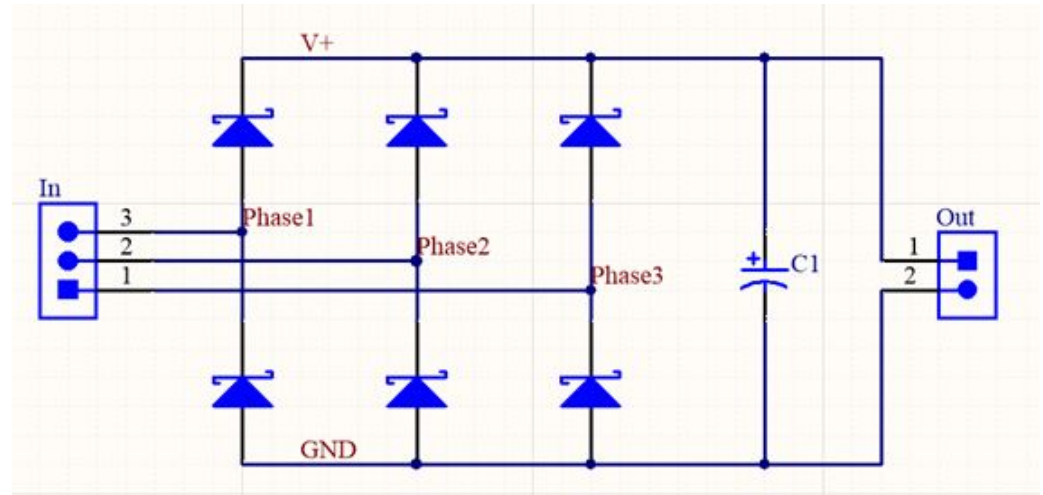
Input/Output Terminals: 2/3  
Hole Screw Terminals



6.9cm
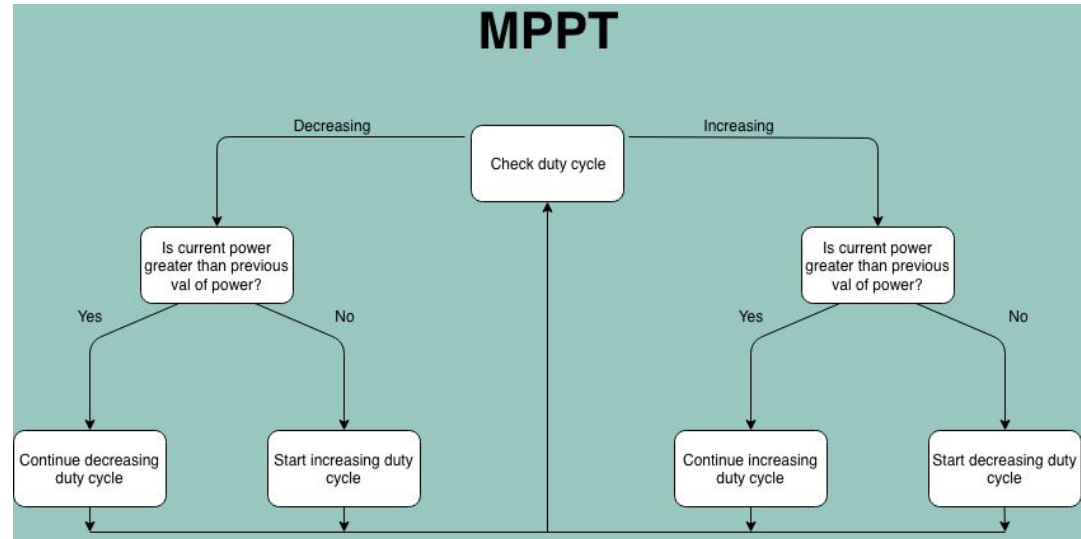
# Control 1

- **MPPT**: Using perturb and observe method to maximize power
- Everytime interrupt trigger mppt() function, compare current power to old power
- If power increased or equal to previous val, continue doing current change of duty cycle, else do the opposite




## Control 2

- **Wind Sensor:** Measure voltage from potentiometer
- Choose the voltage of the potentiometer when it is in the middle as reference
- If the potentiometer voltage is greater than reference, then stepper motor rotates clockwise until potentiometer is within  $\pm 0.1$  V of its reference
- If potentiometer voltage is less than reference, stepper motor rotates counter clockwise
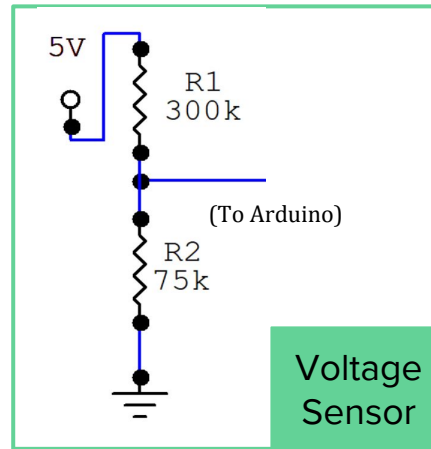
# Sensors

- **Voltage sensor:**

- Accurate to 0.05V
- Voltage divider
  - $R1 = 300k \text{ Ohms}$
  - $R2 = 75k \text{ Ohms}$
  - $R2/(R1+R2)$
- 1/5 ratio




Voltage  
Sensor

- **Current sensor:**


- Accurate to 0.01A
- Shunt with opamp
- Linear relationship
- Expected range 100mA-200mA

- **Wind direction sensor:**

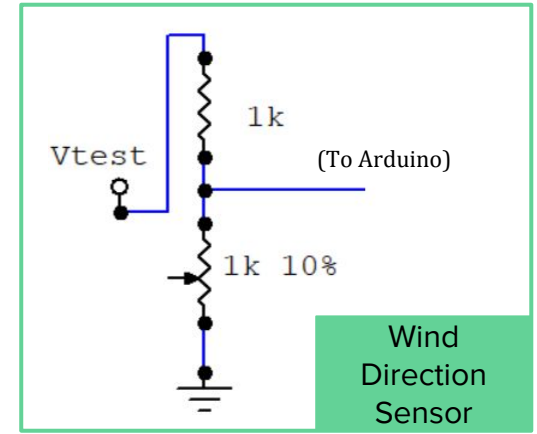- 300 degrees of freedom
- Voltage divider :
  - $R1 = 1k \text{ Ohm resistor}$
  - $R2 = 0-1k \text{ Ohm potentiometer}$
  - 5V input
- Approx. 0-2.5V (0.5 ratio)







Wind  
Direction  
Sensor

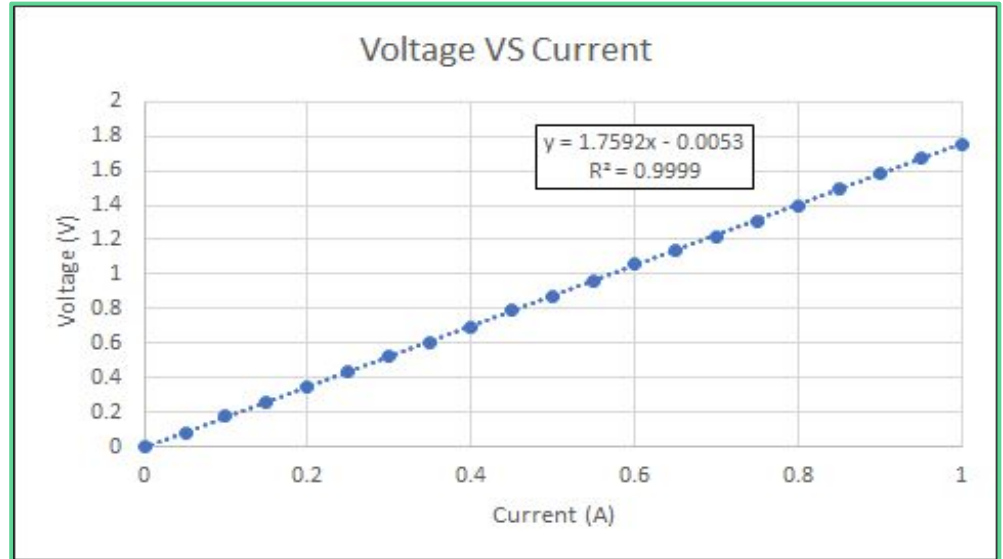



# Simulink models

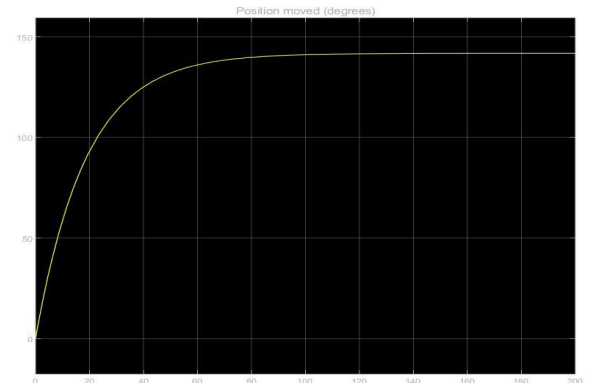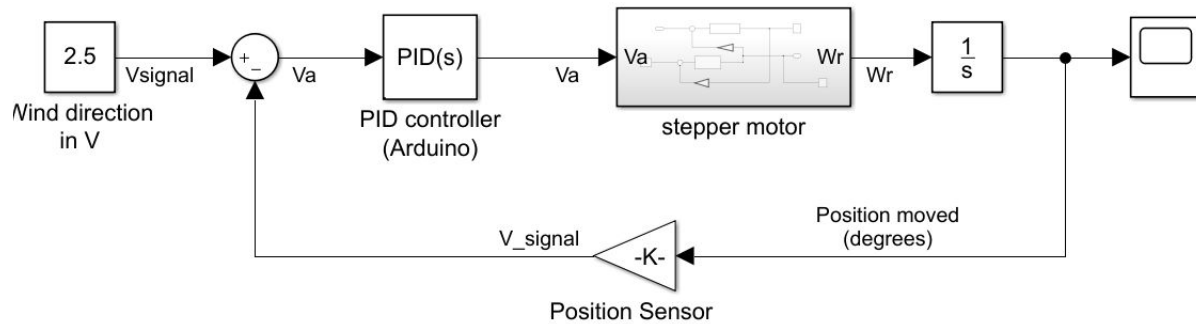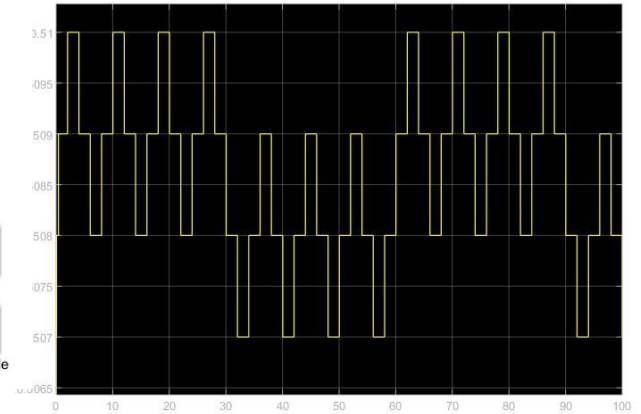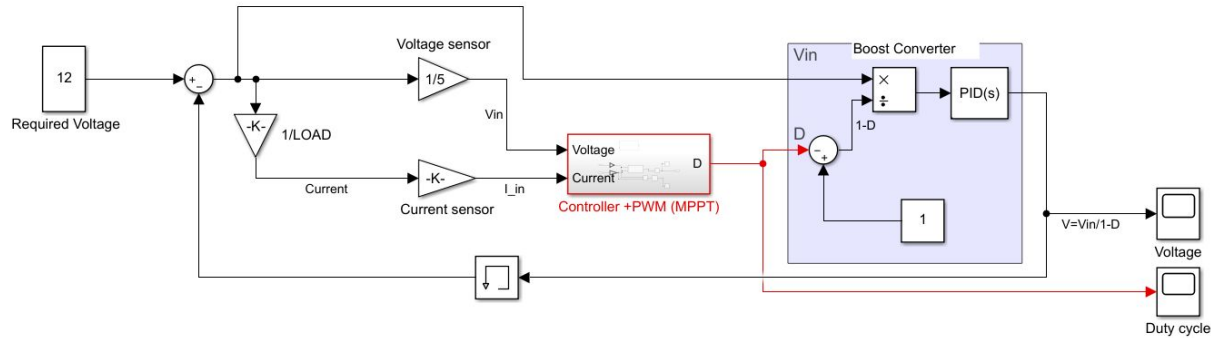

# Bonus

1. Implemented a bluetooth module that allows a connected device to access the arduino's serial port
2. Connect to port through javascript, then read and send data to web server
3. Created a web server using NodeJs, and tunnelled it a public URL, allowing anyone anywhere to access our web interface.
4. Plotted the live data streamed from the Arduino on our web interface.